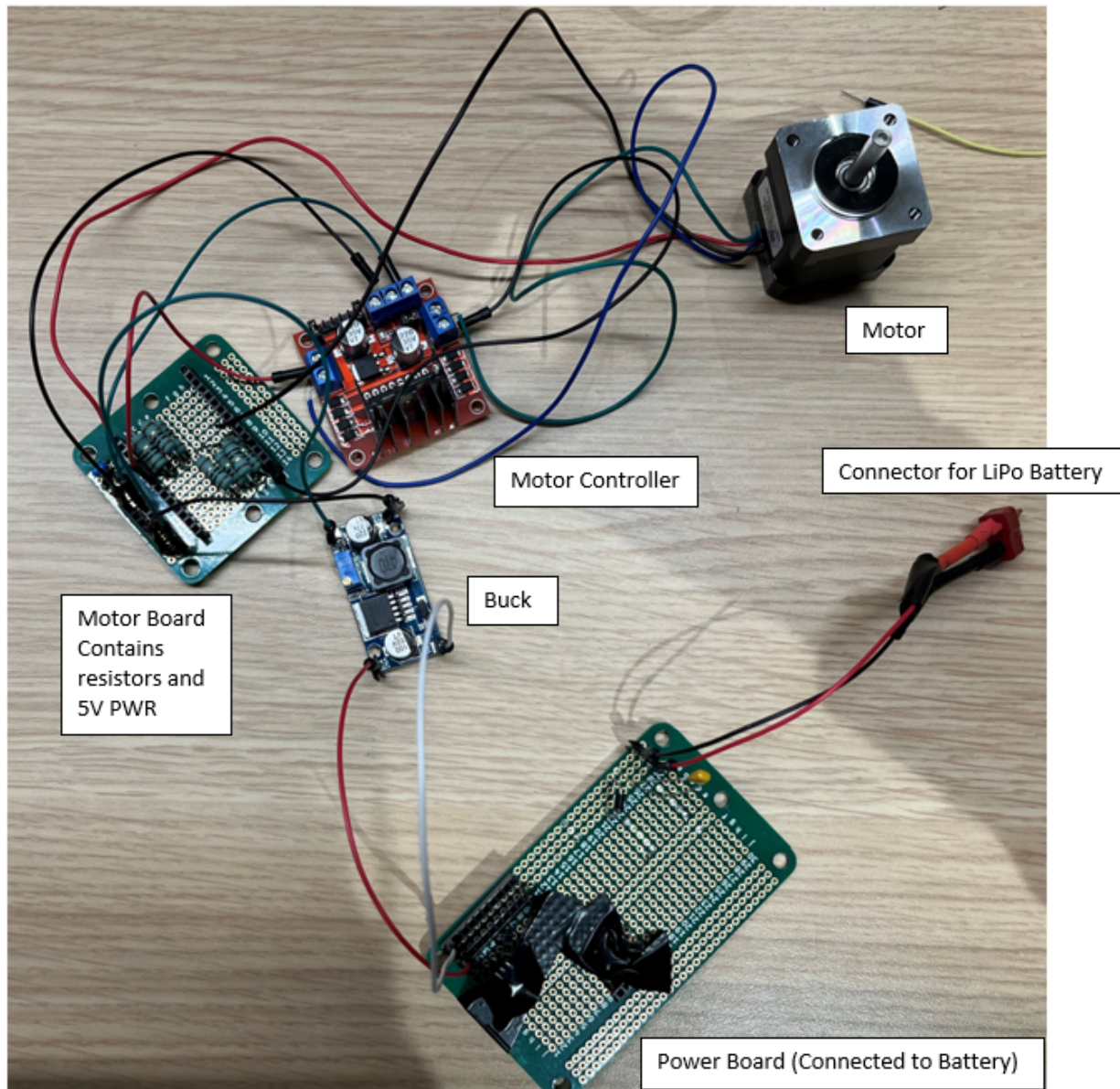
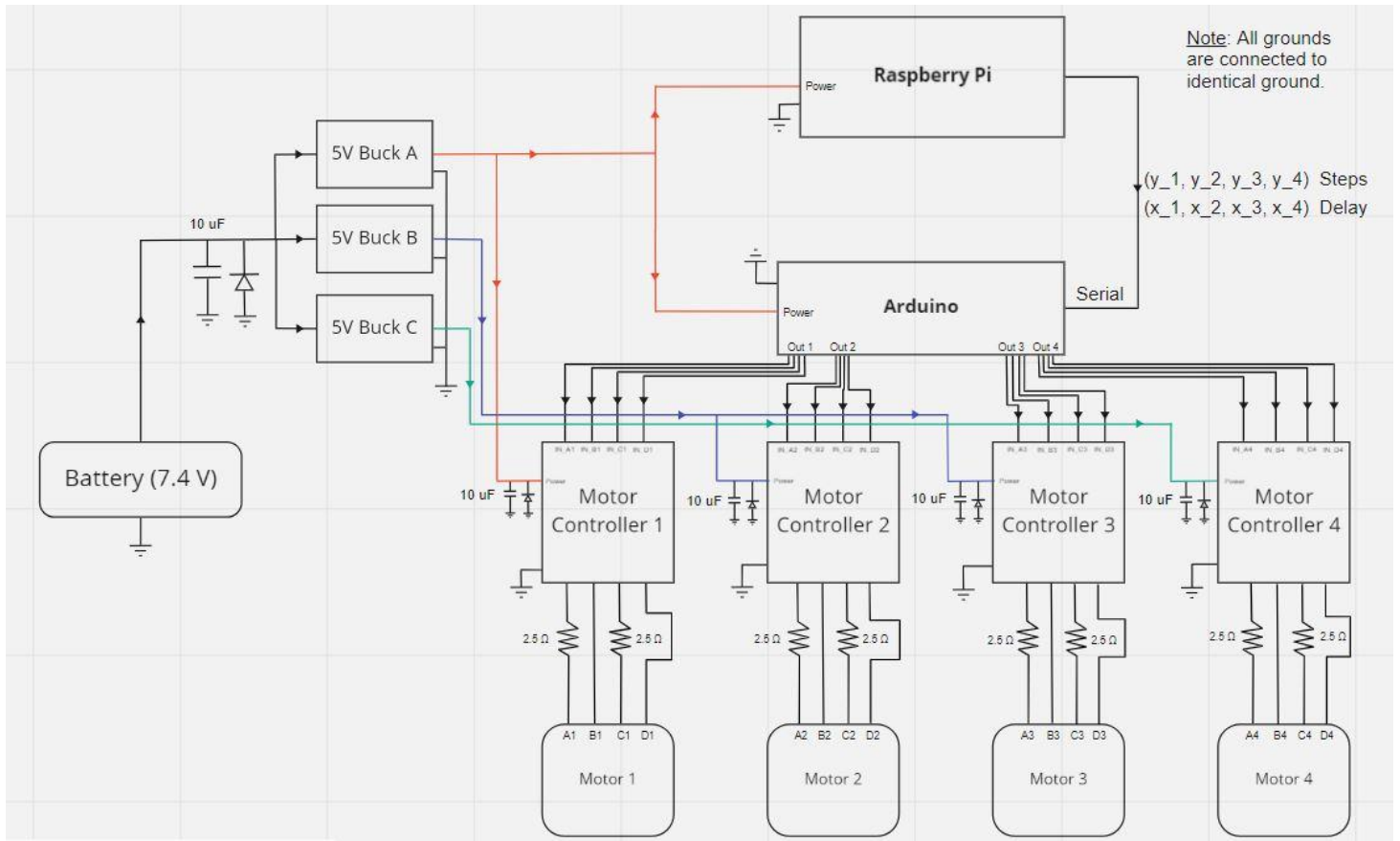


Motor Boards contain resistors for each motor along with 5V PWR and GND rails for each motor controller



Example of 1 Motor Module Connected as described in the Circuit Diagram without connections to Arduino/Raspberry Pi

Circuit Diagram



Note: Colors of the output from the buck does not match with the real wire colors.